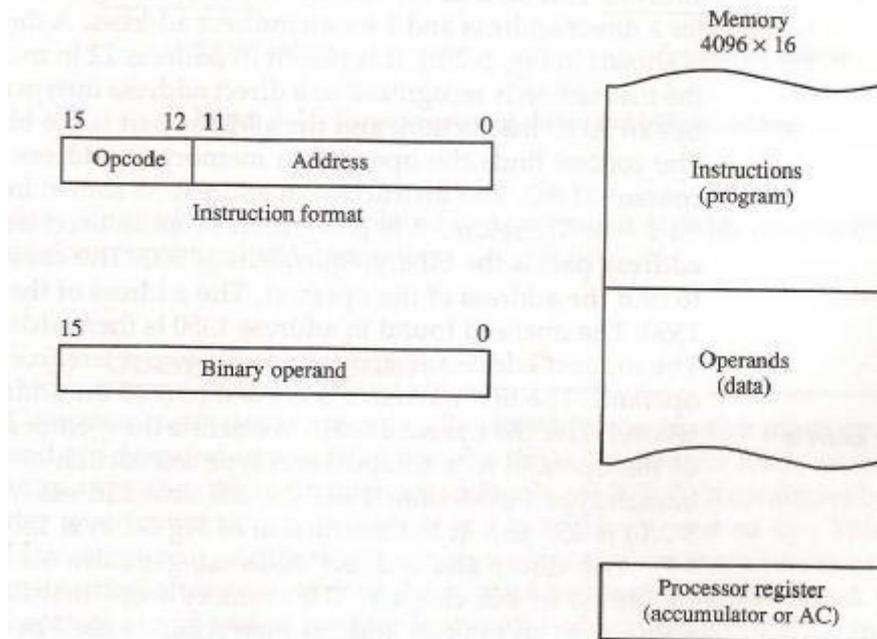


Figure 5-1 Stored program organization.



- Instructions are stored in one section of memory and data in another.
- For a memory unit with 4096 words we need 12 bits to specify an address since $2^{12} = 4096$.
- If we store each instruction code in one 16-bit memory word, we have available four bits for the operation code (abbreviated opcode) to specify one out of 16 possible operations, and 12 bits to specify the address of an operand.
- **Accumulator (AC):**
 - ✓ Computers that have a single-processor register usually assign to it the name accumulator and label it AC.
 - ✓ The operation is performed with the memory operand and the content of AC.

Addressing of Operand:

- Sometimes convenient to use the address bits of an instruction code not as an address but as the actual operand.
- When the second part of an instruction code specifies an operand, the instruction is said to have an **immediate operand**.
- When the second part specifies the address of an operand, the instruction is said to have a **direct address**.
- When second part of the instruction designate an address of a memory word in which the address of the operand is found such instruction have **indirect address**.
- One bit of the instruction code can be used to distinguish between a direct and an indirect address.
- The instruction code format shown in Fig. 5-2(a). It consists of a 3-bit operation code, a 12-bit address, and an indirect address mode bit designated by I. The mode bit is 0 for a direct address and 1 for an indirect address.

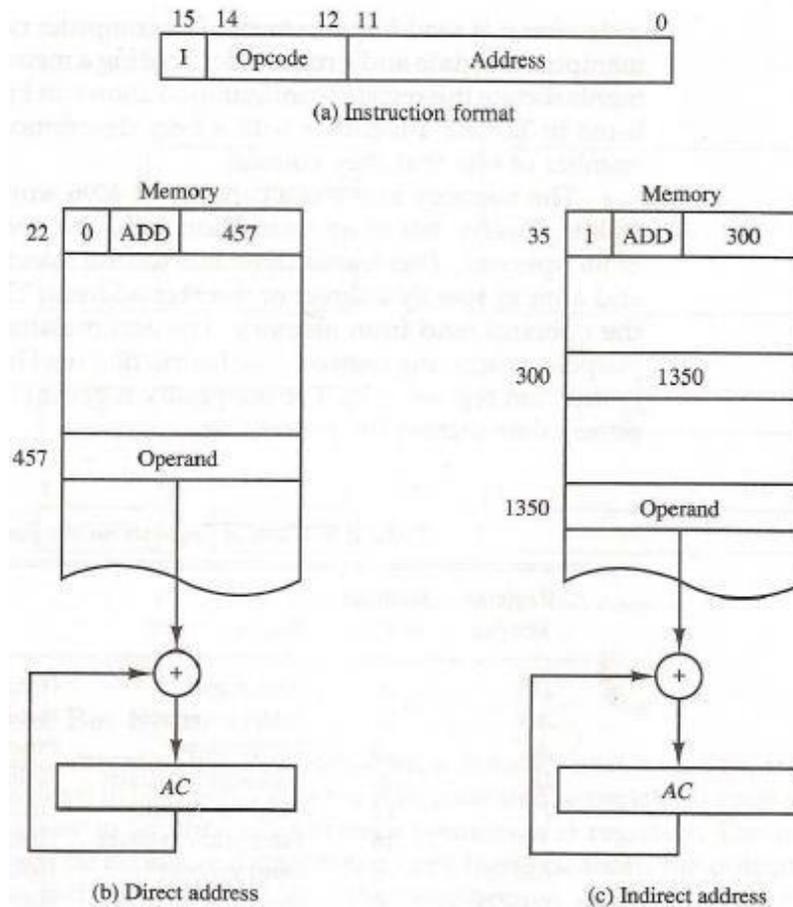


Figure 5-2 Demonstration of direct and indirect address.

- A direct address instruction is shown in Fig. 5-2(b).
- It is placed in address 22 in memory. The I bit is 0, so the instruction is recognized as a direct address instruction. The opcode specifies an ADD instruction, and the address part is the binary equivalent of 457.
- The control finds the operand in memory at address 457 and adds it to the content of AC.
- The instruction in address 35 shown in Fig. 5-2(c) has a mode bit $I = 1$.
- Therefore, it is recognized as an indirect address instruction.
- The address part is the binary equivalent of 300. The control goes to address 300 to find the address of the operand. The address of the operand in this case is 1350.
- The operand found in address 1350 is then added to the content of AC.
- The **effective address** to be the address of the operand in a computation-type instruction or the target address in a branch-type instruction.
- Thus the effective address in the instruction of Fig. 5-2(b) is 457 and in the instruction of Fig 5-2(c) is 1350.


2. Computer Registers:

- What is the need for computer registers?
 - ✓ The need of the registers in computer for
 - Instruction sequencing needs a counter to calculate the address of the next instruction after execution of the current instruction is completed (**PC**).
 - Necessary to provide a register in the control unit for storing the instruction code after it is read from memory (**IR**).
 - Needs processor registers for manipulating data (AC and TR) and a register for holding a memory address (**AR**).
- The above requirements dictate the register configuration shown in Fig. 5-3.

- The registers are also listed in Table 5.1 together with a brief description of their function and the number of bits that they contain.

TABLE 5-1 List of Registers for the Basic Computer

Register symbol	Number of bits	Register name	Function
<i>DR</i>	16	Data register	Holds memory operand
<i>AR</i>	12	Address register	Holds address for memory
<i>AC</i>	16	Accumulator	Processor register
<i>IR</i>	16	Instruction register	Holds instruction code
<i>PC</i>	12	Program counter	Holds address of instruction
<i>TR</i>	16	Temporary register	Holds temporary data
<i>INPR</i>	8	Input register	Holds input character
<i>OUTR</i>	8	Output register	Holds output character

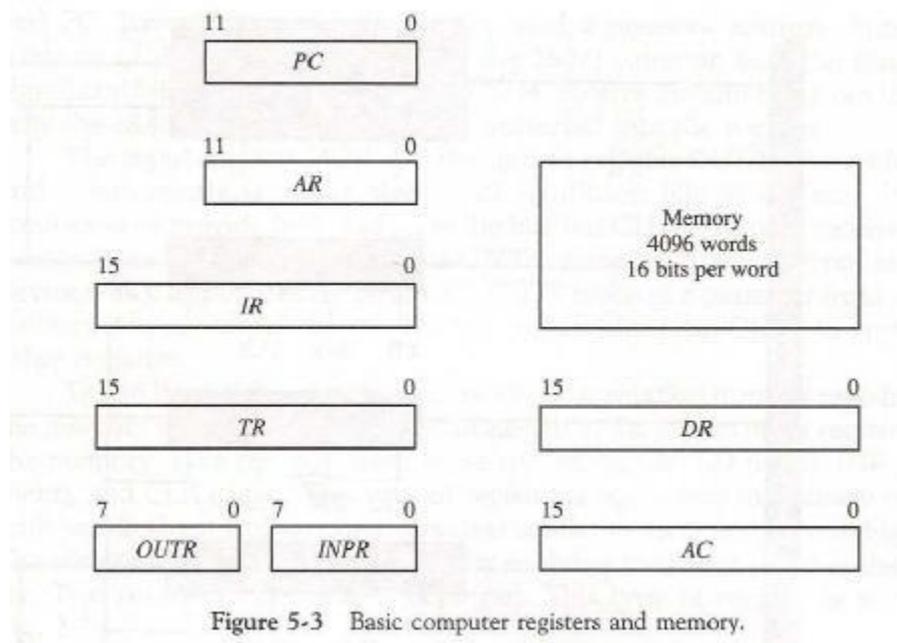

- The data register (DR) holds the operand read from memory.
- The accumulator (AC) register is a general purpose processing register.
- The instruction read from memory is placed in the instruction register (IR).
- The temporary register (TR) is used for holding temporary data during the processing.
- The memory address register (AR) has 12 bits since this is the width of a memory address.
- The program counter (PC) also has 12 bits and it holds the address of the next instruction to be read from memory after the current instruction is executed.
- Two registers are used for input and output.
 - The input register (INPR) receives an 8-bit character from an input device.
 - The output register (OUTR) holds an 8-bit character for an output device.

Common Bus System:

- The basic computer has eight registers, a memory unit, and a control unit
- Paths must be provided to transfer information from one register to another and between memory and registers.
- A more efficient scheme for transferring information in a system with many registers is to use a common bus.
- The connection of the registers and memory of the basic computer to a common bus system is shown in Fig. 5-4.
- The outputs of seven registers and memory are connected to the common bus.

- The specific output that is selected for the bus lines at any given time is determined from the binary value of the selection variables S_2 , S_1 , and S_0 .
- The number along each output shows the decimal equivalent of the required binary selection.
- For example, the number along the output of DR is 3. The 16-bit outputs of DR are placed on the bus lines when $S_2S_1S_0 = 011$.

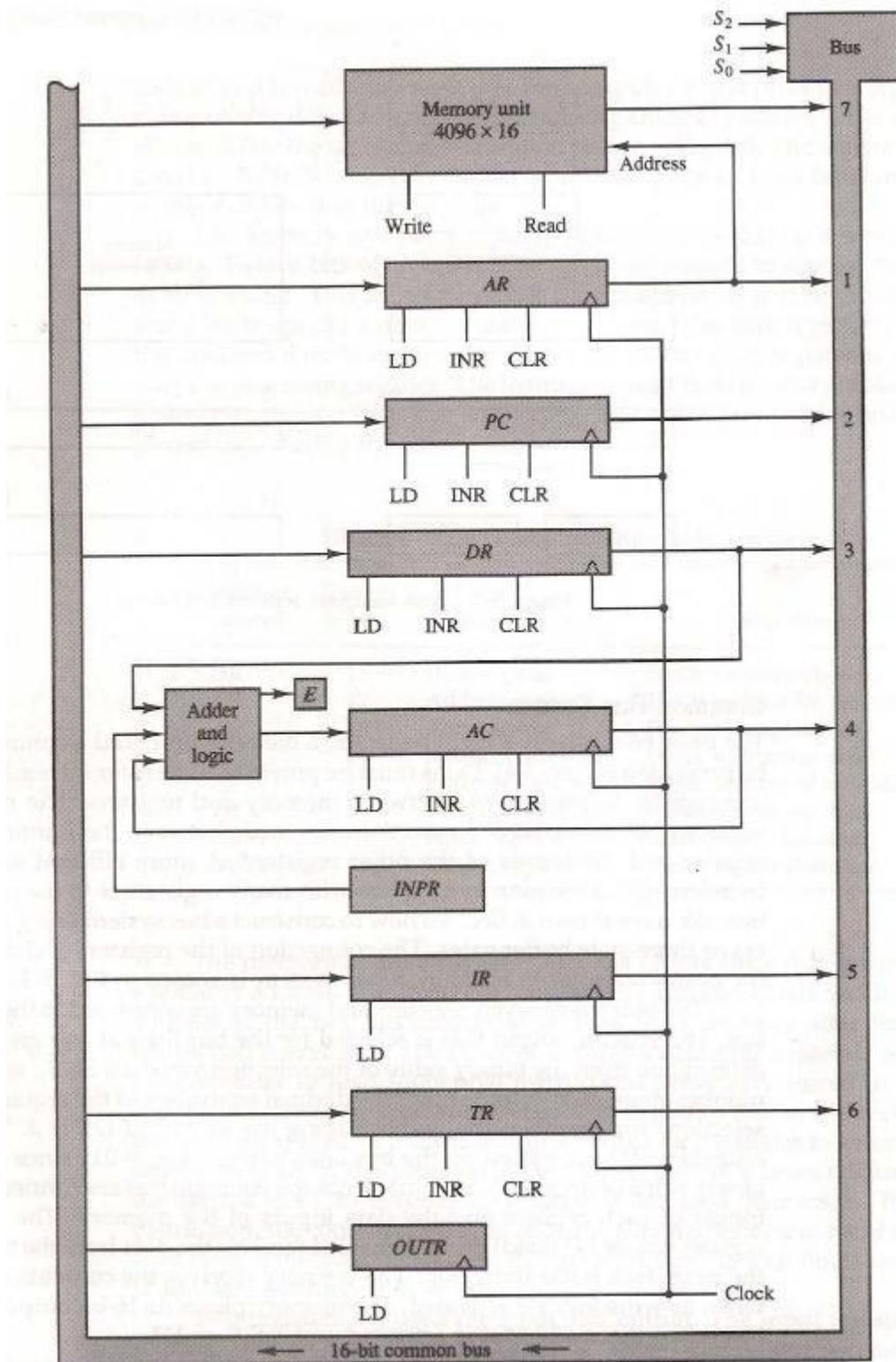


Figure 5-4 Basic computer registers connected to a common bus.


- The lines from the common bus are connected to the inputs of each register and the data inputs of the memory.

- The particular register whose LD (load) input is enabled receives the data from the bus during the next clock pulse transition.
- The memory receives the contents of the bus when its write input is activated.
- The memory places its 16-bit output onto the bus when the read input is activated and $S_2S_1S_0 = 111$.
- Two registers, AR and PC, have 12 bits each since they hold a memory address.
- When the contents of AR or PC are applied to the 16-bit common bus, the four most significant bits are set to 0's.
- When AR or PC receives information from the bus, only the 12 least significant bits are transferred into the register.
- The input register INPR and the output register OUTR have 8 bits each.
- They communicate with the eight least significant bits in the bus.
- INPR is connected to provide information to the bus but OUTR can only receive information from the bus.
- This is because INPR receives a character from an input device which is then transferred to AC.
- OUTR receives a character from AC and delivers it to an output device.
- Five registers have three control inputs: LD (load), INR (increment), and CLR (clear).
- This type of register is equivalent to a binary counter with parallel load and synchronous clear.
- Two registers have only a LD input.
- The input data and output data of the memory are connected to the common bus, but the memory address is connected to AR.
- Therefore, AR must always be used to specify a memory address.
- The 16 inputs of AC come from an adder and logic circuit. This circuit has three sets of inputs.
 - One set of 16-bit inputs come from the outputs of AC.
 - Another set of 16-bit inputs come from the data register DR.
 - The result of an addition is transferred to AC and the end carry-out of the addition is transferred to flip-flop E (extended AC bit).
 - A third set of 8-bit inputs come from the input register INPR.
- The content of any register can be applied onto the bus and an operation can be performed in the adder and logic circuit during the same clock cycle.
- For example, the two microoperations $DR \square AC$ and $AC \square DR$ can be executed at the same time.
- This can be done by placing the content of AC on the bus (with $S_2S_1S_0 = 100$), enabling the LD (load) input of DR, transferring the content of DR through the adder and logic circuit into AC, and enabling the LD (load) input of AC, all during the same clock cycle.

3. Computer Instructions:

- The basic computer has three instruction code formats, as shown in Fig. 5-5. Each format has 16 bits.

Figure 5-5 Basic computer instruction formats.

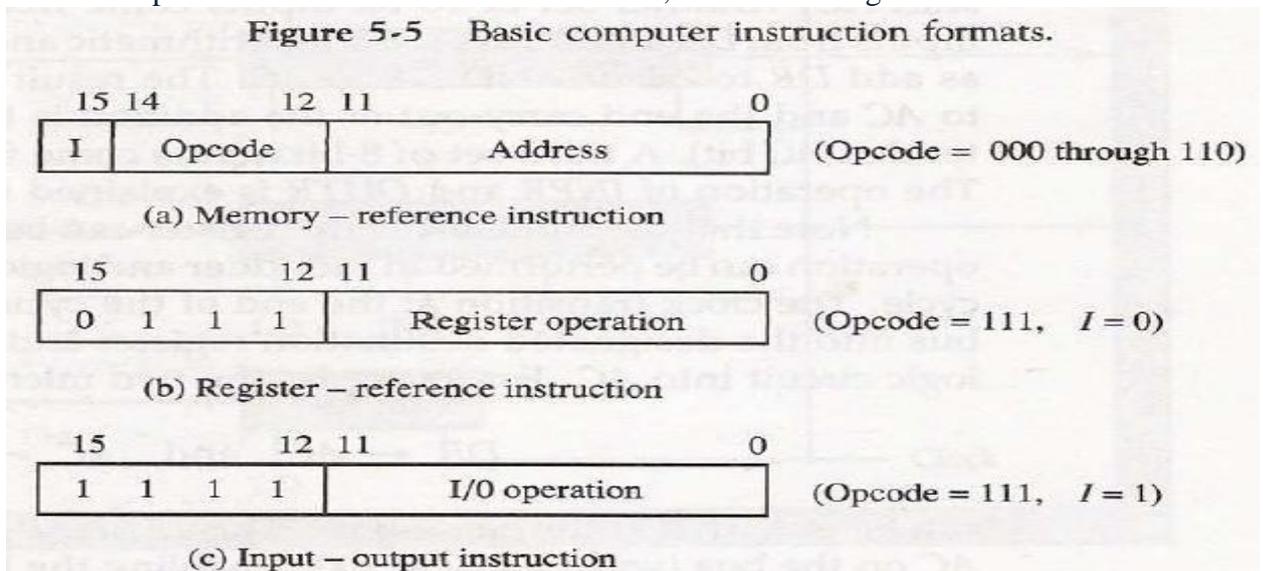

- The operation code (opcode) part of the instruction contains three bits and the meaning of the remaining 13 bits depends on the operation code encountered.
- A memory-reference instruction uses 12 bits to specify an address and one bit to specify the addressing mode *I*.
- *I* is equal to 0 for direct address and to 1 for indirect address.
- The register-reference instructions are recognized by the operation code 1.11 with a 0 in the leftmost bit (bit 15) of the instruction.
- A register-reference instruction specifies an operation on the AC register. So an operand from memory is not needed. Therefore, the other 12 bits are used to specify the operation to be executed.
- An input—output instruction does not need a reference to memory and is recognized by the operation code 111 with a 1 in the leftmost bit of the instruction.
- The remaining 12 bits are used to specify the type of input—output operation.
- The instructions for the computer are listed in Table 5-2.

TABLE 5-2 Basic Computer Instructions

Symbol	Hexadecimal code		Description
	<i>I</i> = 0	<i>I</i> = 1	
AND	0xxx	8xxx	AND memory word to AC
ADD	1xxx	9xxx	Add memory word to AC
LDA	2xxx	Axxx	Load memory word to AC
STA	3xxx	Bxxx	Store content of AC in memory
BUN	4xxx	Cxxx	Branch unconditionally
BSA	5xxx	Dxxx	Branch and save return address
ISZ	6xxx	Exxx	Increment and skip if zero
CLA	7800		Clear AC
CLE	7400		Clear <i>E</i>
CMA	7200		Complement AC
CME	7100		Complement <i>E</i>
CIR	7080		Circulate right AC and <i>E</i>
CIL	7040		Circulate left AC and <i>E</i>
INC	7020		Increment AC
SPA	7010		Skip next instruction if AC positive
SNA	7008		Skip next instruction if AC negative
SZA	7004		Skip next instruction if AC zero
SZE	7002		Skip next instruction if <i>E</i> is 0
HLT	7001		Halt computer
INP	F800		Input character to AC
OUT	F400		Output character from AC
SKI	F200		Skip on input flag
SKO	F100		Skip on output flag
ION	F080		Interrupt on
IOF	F040		Interrupt off

- The symbol designation is a three-letter word and represents an abbreviation intended for programmers and users.
- The hexadecimal code is equal to the equivalent hexadecimal number of the binary code used for the instruction.

Instruction Set Completeness:

- A computer should have a set of instructions so that the user can construct machine language programs to evaluate any function.
- The set of instructions are said to be complete if the computer includes a sufficient number of instructions in each of the following categories:
 - Arithmetic, logical, and shift instructions
 - Data Instructions (for moving information to and from memory and processor registers)
 - Program control or Branch
 - Input and output instructions
- There is one arithmetic instruction, ADD, and two related instructions, complement AC(CMA) and increment AC(INC). With these three instructions we can add and subtract binary numbers when negative numbers are in signed-2's complement representation.
- The circulate instructions, CIR and CIL; can be used for arithmetic shifts as well as any other type of shifts desired.
- There are three logic operations: AND, complement AC (CMA), and clear AC(CLA). The AND and complement provide a NAND operation.
- Moving information from memory to AC is accomplished with the load AC (LDA) instruction. Storing information from AC into memory is done with the store AC (STA) instruction.
- The branch instructions BUN, BSA, and ISZ, together with the four skip instructions, provide capabilities for program control and checking of status conditions.
- The input (INP) and output (OUT) instructions cause information to be transferred between the computer and external devices.

4. Timing and Control:

- The timing for all registers in the basic computer is controlled by a master clock generator.
- The clock pulses are applied to all flip-flops and registers in the system, including the flip-flops and registers in the control unit.
- The clock pulses do not change the state of a register unless the register is enabled by a control signal.
- The control signals are generated in the control unit and provide control inputs for the multiplexers in the common bus, control inputs in processor registers, and microoperations for the accumulator.
- There are two major types of control organization:
 - Hardwired control
 - Microprogrammed control
- The differences between hardwired and microprogrammed control are

Hardwired control	Microprogrammed control
✓ The control logic is implemented with gates, flip-flops, decoders, and other digital circuits.	✓ The control information is stored in a control memory. The control memory is programmed to initiate the required sequence of microoperations.
✓ The advantage that it can be optimized to produce a fast mode of operation.	✓ Compared with the hardwired control operation is slow.
✓ Requires changes in the wiring among the various components if the design has to be modified or changed.	✓ Required changes or modifications can be done by updating the microprogram in control memory.

- The block diagram of the hardwired control unit is shown in Fig. 5-6.
- It consists of two decoders, a sequence counter, and a number of control logic gates.
- An instruction read from memory is placed in the instruction register (IR). It is divided into three parts: The I bit, the operation code, and bits 0 through 11.
- The operation code in bits 12 through 14 are decoded with a 3 x 8 decoder. The eight outputs of the decoder are designated by the symbols D_0 through D_7 .
- Bit 15 of the instruction is transferred to a flip-flop designated by the symbol I.
- Bits 0 through 11 are applied to the control logic gates.
- The 4-bit sequence counter can count in binary from 0 through 15.

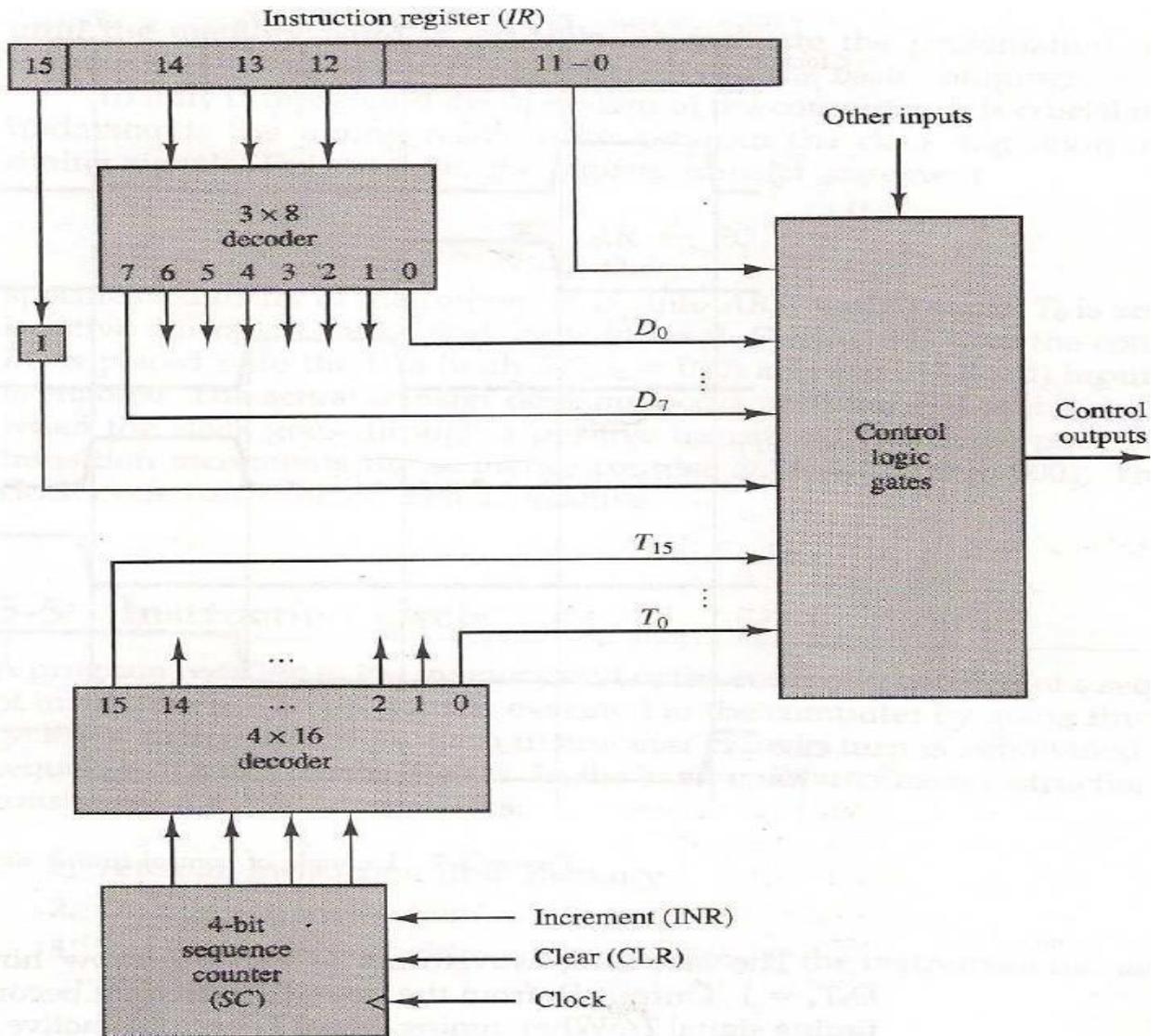



Figure 5-6 Control unit of basic computer.

- The outputs of the counter are decoded into 16 timing signals T_0 through T_{15} .
- The sequence counter SC can be incremented or cleared synchronously.
- The counter is incremented to provide the sequence of timing signals out of the 4 x 16 decoder.
- As an example, consider the case where SC is incremented to provide timing signals T_0 , T_1 , T_2 , T_3 and T_4 in sequence. At time T_4 , SC is cleared to 0 if decoder output D_3 is active.
- This is expressed symbolically by the statement

$D_3T_4: SC \square 0$

- The timing diagram of Fig. 5-7 shows the time relationship of the control signals.

- The sequence counter SC responds to the positive transition of the clock.
- Initially, the CLR input of SC is active. The first positive transition of the clock clears SC to 0, which in turn activates the timing signal T_0 out of the decoder. T_0 is active during one clock cycle.
- SC is incremented with every positive clock transition, unless its CLR input is active.
- This produces the sequence of timing signals T_0, T_1, T_2, T_3, T_4 and so on, as shown in the diagram.
- The last three waveforms in Fig.5-7 show how SC is cleared when $D_3T_4 = 1$.
- Output D_3 from the operation decoder becomes active at the end of timing signal T_2 .
- When timing signal T_4 becomes active, the output of the AND gate that implements the control function D_3T_4 becomes active.
- This signal is applied to the CLR input of SC. On the next positive clock transition (the one marked T_4 in the diagram) the counter is cleared to 0.
- This causes the timing signal T_0 to become active instead of T_5 that would have been active if SC were incremented instead of cleared.

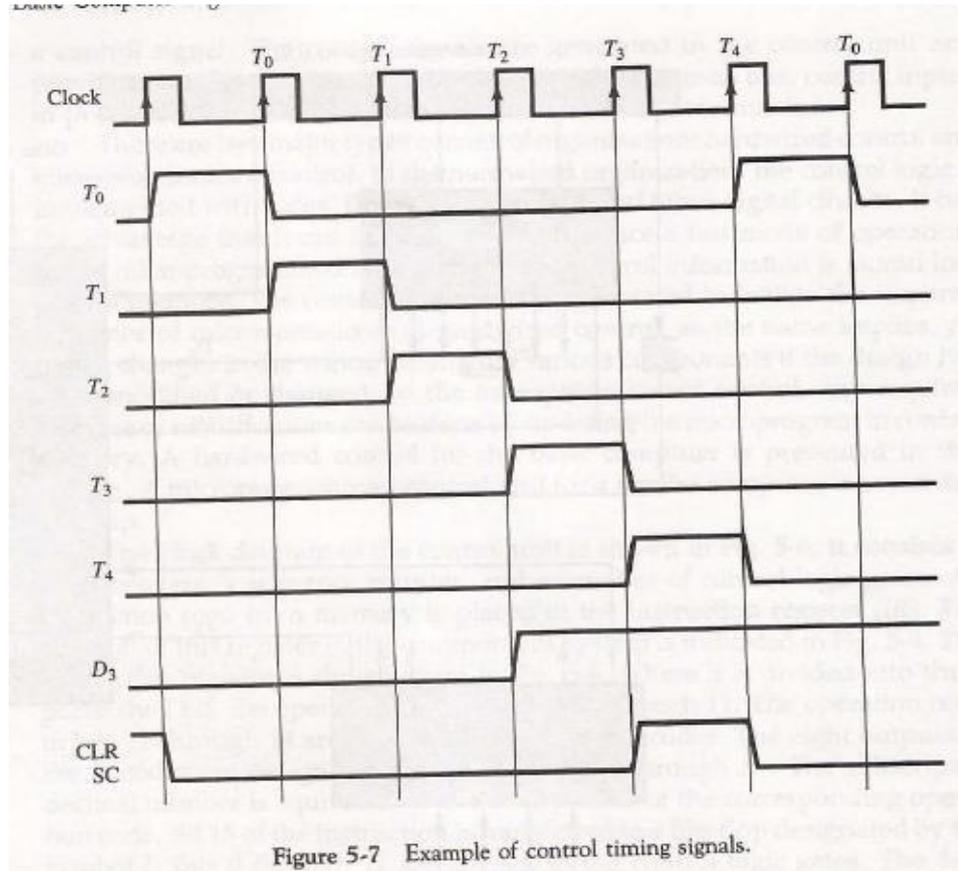

5. Instruction Cycle:

- A program residing in the memory unit of the computer consists of a sequence of instructions.
- The program is executed in the computer by going through a cycle for each instruction.
- Each instruction cycle in turn is subdivided into a sequence of sub cycles or phases.
- In the basic computer each instruction cycle consists of the following phases:
 1. Fetch an instruction from memory.
 2. Decode the instruction.
 3. Read the effective address from memory if the instruction has an indirect address.
 4. Execute the instruction.
- Upon the completion of step 4, the control goes back to step 1 to fetch, decode, and execute the next instruction.

Fetch and Decode:

- Initially, the program counter PC is loaded with the address of the first instruction in the program.

- The sequence counter SC is cleared to 0, providing a decoded timing signal T_0 .
- The microoperations for the fetch and decode phases can be specified by the following register transfer statements.

$T_0: AR \leftarrow PC$
 $T_1: IR \leftarrow M[AR], PC \leftarrow PC + 1$
 $T_2: D_0, \dots, D_7 \leftarrow \text{Decode } IR(12-14), AR \leftarrow IR(0-11), I \leftarrow IR(15)$

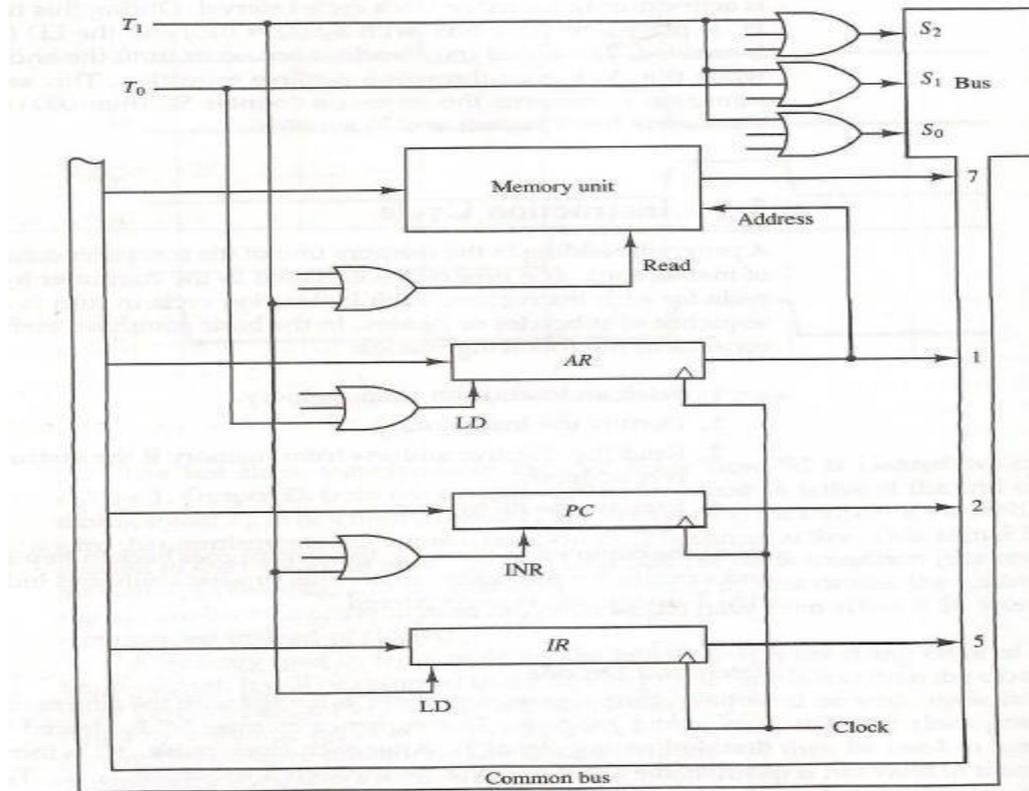


Figure 5-8 Register transfers for the fetch phase.

- Figure 5-8 shows how the first two register transfer statements are implemented in the bus system.
- To provide the data path for the transfer of PC to AR we must apply timing signal T_0 to achieve the following connection:
 - Place the content of PC onto the bus by making the bus selection inputs S_2, S_1, S_0 equal to 010.
 - Transfer the content of the bus to AR by enabling the LD input of AR.
- In order to implement the second statement it is necessary to use timing signal T_1 to provide the following connections in the bus system.
 - Enable the read input of memory.
 - Place the content of memory onto the bus by making $S_2S_1S_0=111$.
 - Transfer the content of the bus to IR by enabling the LD input of IR.
 - Increment PC by enabling the INR input of PC.
- Multiple input OR gates are included in the diagram because there are other control functions that will initiate similar operations.

Determine the Type of Instruction:

- The timing signal that is active after the decoding is T_3 .
- During time T_3 , the control unit determine the type of instruction that was read from the memory.
- The flowchart of fig.5-9 shows the initial configurations for the instruction cycle and also how the control determines the instruction cycle type after the decoding.
- Decoder output D_7 is equal to 1 if the operation code is equal to binary 111.
- If $D_7=1$, the instruction must be a register-reference or input-output type.
- If $D_7 = 0$, the operation code must be one of the other seven values 000 through 110, specifying a memory-reference instruction.

- Control then inspects the value of the first bit of the instruction, which is now available in flip-flop I.
- If $D_7 = 0$ and $I = 1$, indicates a memory-reference instruction with an indirect address. So it is then necessary to read the effective address from memory.
- If $D_7 = 0$ and $I = 0$, indicates a memory-reference instruction with a direct address.
- If $D_7 = 1$ and $I = 0$, indicates a register-reference instruction.
- If $D_7 = 0$ and $I = 1$, indicates an input-output instruction.
- The three instruction types are subdivided into four separate paths.
- The selected operation is activated with the clock transition associated with timing signal T_3 .
- This can be symbolized as follows:

$D_7 I T_3$: $AR \leftarrow M[AR]$
 $D_7 I' T_3$: Nothing
 $D_7 I' T_3$: Execute a register-reference instruction
 $D_7 I T_3$: Execute an input-output instruction

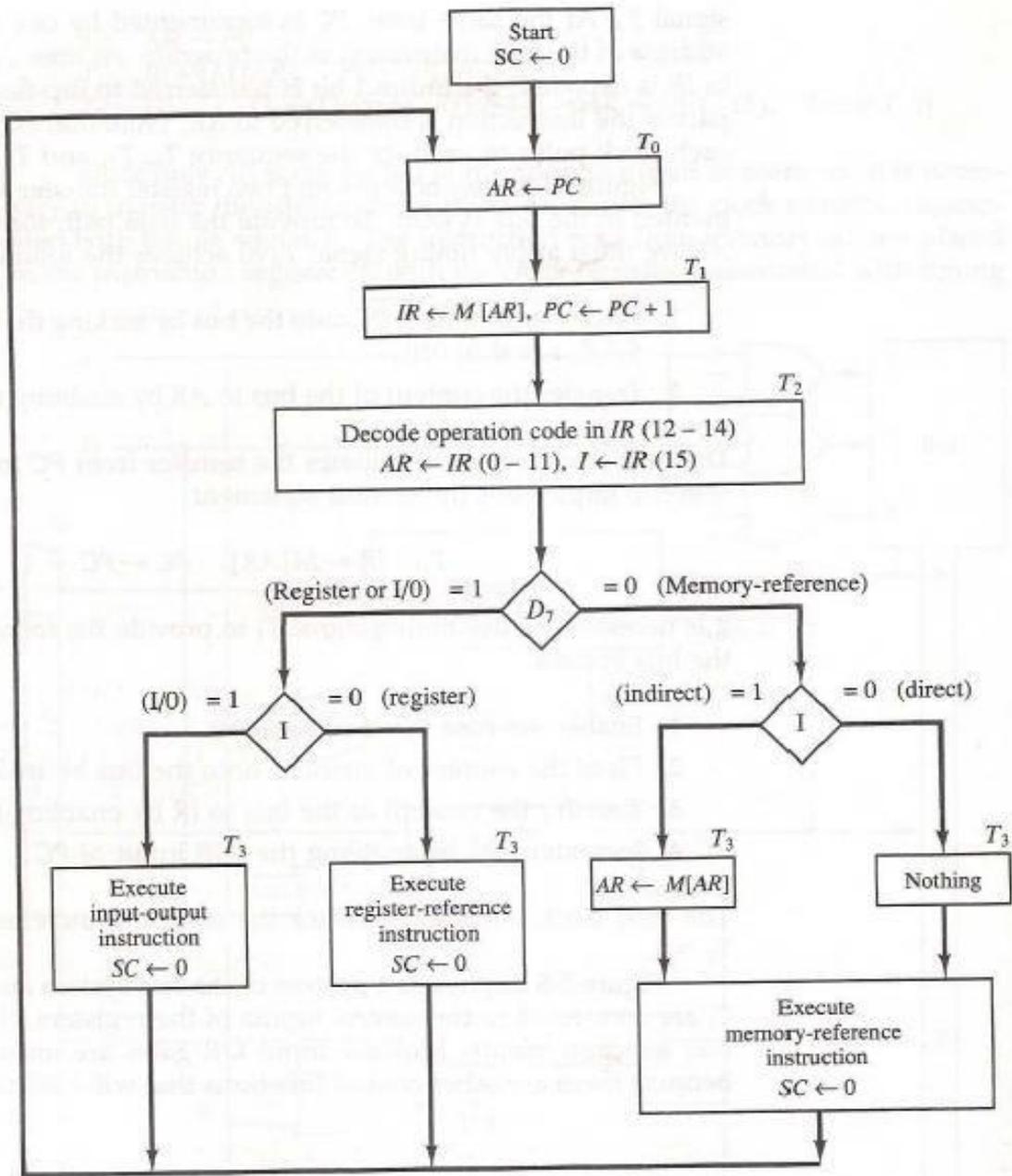


Figure 5-9 Flowchart for instruction cycle (initial configuration).

Register-Reference Instructions:

- Register-reference instructions are recognized by the control when $D_7 = 1$ and $I=0$.
- These instructions use bits 0 through 11 of the instruction code to specify one of 12 instructions.
- These 12 bits are available in IR (0-11).
- The control functions and microoperations for the register-reference instructions are listed in Table 5-3.
- These instructions are executed with the clock transition associated with timing variable T_3 .
- Control function needs the Boolean relation $D_7I'T_3$, which we designate for convenience by the symbol r .
- By assigning the symbol B_i to bit i of IR, all control functions can be simply denoted by rB_i .

TABLE 5-3 Execution of Register-Reference Instructions

$D_7I'T_3 = r$ (common to all register-reference instructions)			
$IR(i) = B_i$ [bit in IR(0-11) that specifies the operation]			
	r :	$SC \leftarrow 0$	Clear SC
CLA	rB_{11} :	$AC \leftarrow 0$	Clear AC
CLE	rB_{10} :	$E \leftarrow 0$	Clear E
CMA	rB_9 :	$AC \leftarrow \overline{AC}$	Complement AC
CME	rB_8 :	$E \leftarrow \overline{E}$	Complement E
CIR	rB_7 :	$AC \leftarrow \text{shr } AC, AC(15) \leftarrow E, E \leftarrow AC(0)$	Circulate right
CIL	rB_6 :	$AC \leftarrow \text{shl } AC, AC(0) \leftarrow E, E \leftarrow AC(15)$	Circulate left
INC	rB_5 :	$AC \leftarrow AC + 1$	Increment AC
SPA	rB_4 :	If $(AC(15) = 0)$ then $(PC \leftarrow PC + 1)$	Skip if positive
SNA	rB_3 :	If $(AC(15) = 1)$ then $(PC \leftarrow PC + 1)$	Skip if negative
SZA	rB_2 :	If $(AC = 0)$ then $PC \leftarrow PC + 1$	Skip if AC zero
SZE	rB_1 :	If $(E = 0)$ then $(PC \leftarrow PC + 1)$	Skip if E zero
HLT	rB_0 :	$S \leftarrow 0$ (S is a start-stop flip-flop)	Halt computer

- For example, the instruction CLA has the hexadecimal code 7800, which gives the binary equivalent 0111 1000 0000 0000. The first bit is a zero and is equivalent to I' .
- The next three bits constitute the operation code and are recognized from decoder output D_7 .
- Bit 11 in IR is 1 and is recognized from B_{11} . The control function that initiates the microoperation for this instruction is $D_7I'T_3 B_{11} = rB_{11}$.
- The execution of a register-reference instruction is completed at time T_3 .
- The sequence counter SC is cleared to 0 and the control goes back to fetch the next instruction with timing signal T_0 .
- The first seven register-reference instructions perform clear, complement, circular shift, and increment microoperations on the AC or E registers.
- The next four instructions cause a skip of the next instruction in sequence when a stated condition is satisfied. The skipping of the instruction is achieved by incrementing PC once again.
- The condition control statements must be recognized as part of the control conditions.
- The AC is positive when the sign bit in $AC(15) = 0$; it is negative when $AC(15) = 1$. The content of AC is zero ($AC = 0$) if all the flip-flops of the register are zero.
- The HLT instruction clears a start-stop flip-flop S and stops the sequence counter from counting.

6. Memory-Reference Instructions:

- Table 5-4 lists the seven memory-reference instructions.
- The decoded output D_i for $i = 0, 1, 2, 3, 4, 5,$ and 6 from the operation decoder that belongs to each instruction is included in the table.
- The effective address of the instruction is in the address register AR and was placed there during timing signal T_2 when $I = 0$, or during timing signal T_3 when $I = 1$.
- The execution of the memory-reference instructions starts with timing signal T_4 .

- The symbolic description of each instruction is specified in the table in terms of register transfer notation.

TABLE 5-4 Memory-Reference Instructions

Symbol	Operation decoder	Symbolic description
AND	D_0	$AC \leftarrow AC \wedge M[AR]$
ADD	D_1	$AC \leftarrow AC + M[AR], E \leftarrow C_{out}$
LDA	D_2	$AC \leftarrow M[AR]$
STA	D_3	$M[AR] \leftarrow AC$
BUN	D_4	$PC \leftarrow AR$
BSA	D_5	$M[AR] \leftarrow PC, PC \leftarrow AR + 1$
ISZ	D_6	$M[AR] \leftarrow M[AR] + 1,$ If $M[AR] + 1 = 0$ then $PC \leftarrow PC + 1$

AND to AC:

- This is an instruction that performs the AND logic operation on pairs of bits in AC and the memory word specified by the effective address.
- The result of the operation is transferred to AC.
- The microoperations that execute this instruction are:

$$D_0T_4: DR \leftarrow M[AR]$$

$$D_0T_5: AC \leftarrow AC \wedge DR, SC \leftarrow 0$$

ADD to AC:

- This instruction adds the content of the memory word specified by the effective address to the value of AC.
- The sum is transferred into AC and the output carry C_{out} is transferred to the E (extended accumulator) flip-flop.
- The microoperations needed to execute this instruction are

$$D_1T_4: DR \leftarrow M[AR]$$

$$D_1T_5: AC \leftarrow AC + DR, E \leftarrow C_{out}, SC \leftarrow 0$$

LDA: Load to AC

- This instruction transfers the memory word specified by the effective address to AC.
- The microoperations needed to execute this instruction are

$$D_2T_4: DR \leftarrow M[AR]$$

$$D_2T_5: AC \leftarrow DR, SC \leftarrow 0$$

STA: Store AC

- This instruction stores the content of AC into the memory word specified by the effective address.

- Since the output of AC is applied to the bus and the data input of memory is connected to the bus, we can execute this instruction with one microoperation.

$$D_3T_4: M[AR] \leftarrow AC, SC \leftarrow 0$$

BUN: Branch Unconditionally

- This instruction transfers the program to the instruction specified by the effective address.
- The BUN instruction allows the programmer to specify an instruction out of sequence and we say that the program branches (or jumps) unconditionally.
- The instruction is executed with one microoperation:

$$D_4T_4: PC \leftarrow AR, SC \leftarrow 0$$


BSA: Branch and Save Return Address

- This instruction is useful for branching to a portion of the program called a subroutine or procedure.
- When executed, the BSA instruction stores the address of the next instruction in sequence (which is available in PC) into a memory location specified by the effective address.
- The effective address plus one is then transferred to PC to serve as the address of the first instruction in the subroutine.
- This operation was specified with the following register transfer:

$$M[AR] \leftarrow PC, PC \leftarrow AR + 1$$

- A numerical example that demonstrates how this instruction is used with a subroutine is shown in Fig. 5-10.

Figure 5-10 Example of BSA instruction execution.

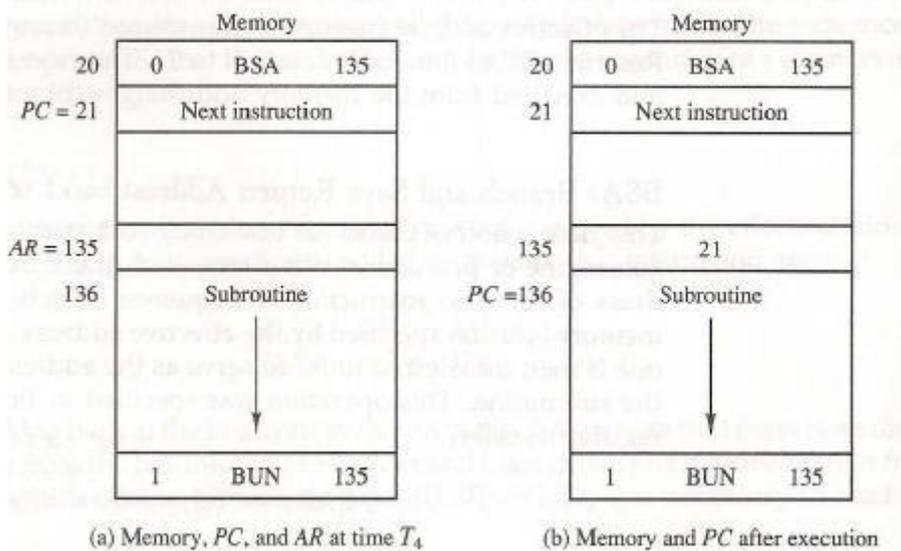

- The BSA instruction is assumed to be in memory at address 20.
- The I bit is 0 and the address part of the instruction has the binary equivalent of 135.
- After the fetch and decode phases, PC contains 21, which is the address of the next instruction in the program (referred to as the return address). AR holds the effective address 135.
- This is shown in part (a) of the figure.
- The BSA instruction performs the following numerical operation:

$$M[135] \leftarrow 21, PC \leftarrow 135 + 1 = 136$$
- The result of this operation is shown in part (b) of the figure.
- The return address 21 is stored in memory location 135 and control continues with the subroutine program starting from address 136.
- The return to the original program (at address 21) is accomplished by means of an indirect BUN instruction placed at the end of the subroutine.

- When this instruction is executed, control goes to the indirect phase to read the effective address at location 135, where it finds the previously saved address 21.
- When the BUN instruction is executed, the effective address 21 is transferred to PC.
- The next instruction cycle finds PC with the value 21, so control continues to execute the instruction at the return address.
- The BSA instruction must be executed with a sequence of two microoperations:

$$D_5T_4: M[AR] \leftarrow PC, AR \leftarrow AR + 1$$

$$D_5T_5: PC \leftarrow AR, SC \leftarrow 0$$

ISZ: Increment and Skip if Zero

- This instruction increment the word specified by the effective address, and if the incremented value is equal to 0, PC is incremented by 1 to skip the next instruction in the program.
- Since it is not possible to increment a word inside the memory, it is necessary to read the word into DR, increment DR, and store the word back into memory.
- This is done with the following sequence of microoperations:

$$D_6T_4: DR \leftarrow M[AR]$$

$$D_6T_5: DR \leftarrow DR + 1$$

$$D_6T_6: M[AR] \leftarrow DR, \text{ if } (DR = 0) \text{ then } (PC \leftarrow PC + 1), SC \leftarrow 0$$

Control Flowchart:

- A flowchart showing all microoperations for the execution of the seven memory-reference instructions is shown in Fig. 5.11.

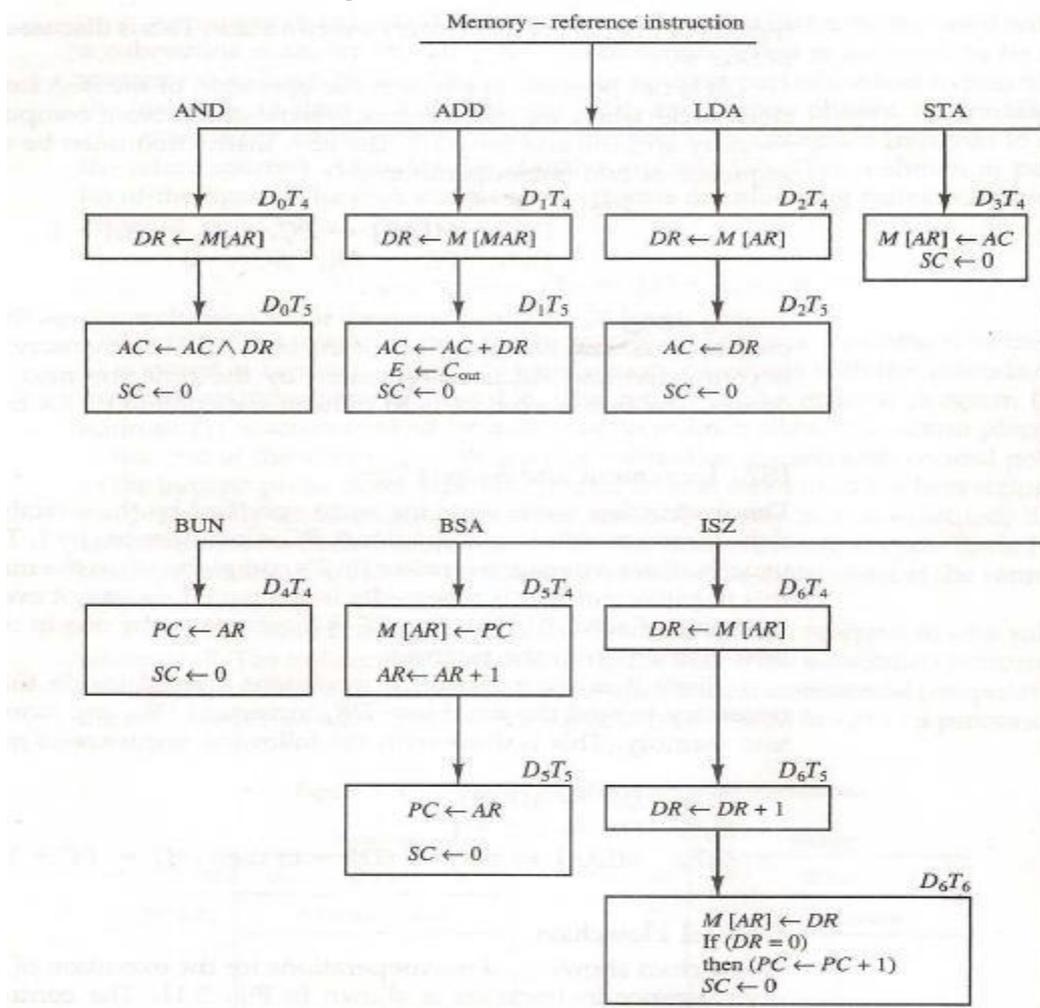


Figure 5-11 Flowchart for memory-reference instructions.


7. Input-Output and Interrupt:

- ❑ Instructions and data stored in memory must come from some input device.
- ❑ Computational results must be transmitted to the user through some output device.
- ❑ To demonstrate the most basic requirements for input and output communication, we will use as an illustration a terminal unit with a keyboard and printer.

Input-Output Configuration:

- ❑ The terminal sends and receives serial information.
- ❑ Each quantity of information has eight bits of an alphanumeric code.
- ❑ The serial information from the keyboard is shifted into the input register INPR.
- ❑ The serial information for the printer is stored in the output register OTR.
- ❑ These two registers communicate with a communication interface serially and with the AC in parallel.
- ❑ The input—output configuration is shown in Fig. 5-12.

Figure 5-12 Input-output configuration.

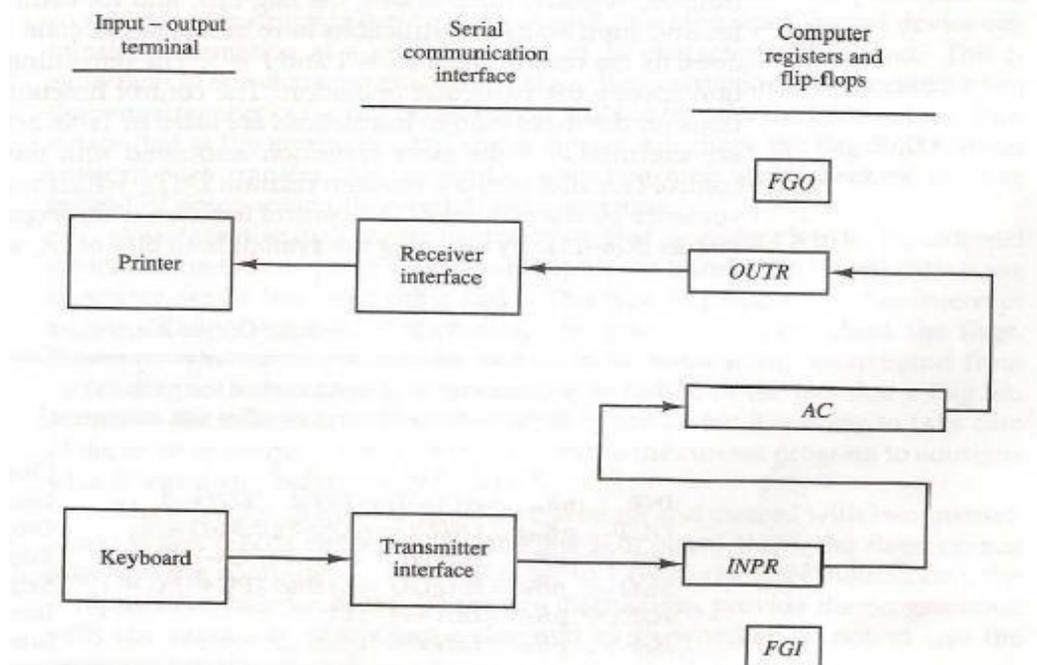

- ❑ The input register INPR consists of eight bits and holds alphanumeric input information.
- ❑ The 1-bit input flag FGI is a control flip-flop.
- ❑ The flag bit is set to 1 when new information is available in the input device and is cleared to 0 when the information is accepted by the computer.
- ❑ The output register OTR works similarly but the direction of information flow is reversed.
- ❑ Initially, the output flag FGO is set to 1.
- ❑ The computer checks the flag bit; if it is 1, the information from AC is transferred in parallel to OTR and FGO is cleared to 0.
- ❑ The output device accepts the coded information, prints the corresponding character, and when the operation is completed, it sets FGO to 1.

Input-Output Instructions:

- ❑ Input and output instructions are needed for transferring information to and from AC register, for checking the flag bits, and for controlling the interrupt facility.
- ❑ Input-output instructions have an operation code 1111 and are recognized by the control when $D7 = 1$ and $I = 1$.
- ❑ The remaining bits of the instruction specify the particular operation.


- The control functions and microoperations for the input-output instructions are listed in Table 5-5.

$D_7IT_3 = p$ (common to all input-output instructions)		
$IR(i) = B_i$ [bit in $IR(6-11)$ that specifies the instruction]		
	p :	$SC \leftarrow 0$ Clear SC
INP	pB_{11} :	$AC(0-7) \leftarrow INPR, FGI \leftarrow 0$ Input character
OUT	pB_{10} :	$OUTR \leftarrow AC(0-7), FGO \leftarrow 0$ Output character
SKI	pB_9 :	If ($FGI = 1$) then ($PC \leftarrow PC + 1$) Skip on input flag
SKO	pB_8 :	If ($FGO = 1$) then ($PC \leftarrow PC + 1$) Skip on output flag
ION	pB_7 :	$IEN \leftarrow 1$ Interrupt enable on
IOF	pB_6 :	$IEN \leftarrow 0$ Interrupt enable off

- These instructions are executed with the clock transition associated with timing signal T_3 .
- Each control function needs a Boolean relation D_7IT_3 , which we designate for convenience by the symbol p .
- The control function is distinguished by one of the bits in IR (6-11).
- By assigning the symbol B_i to bit i of IR , all control functions can be denoted by pB_i for $i = 6$ through 11.
- The sequence counter SC is cleared to 0 when $p = D_7IT_3 = 1$.
- The last two instructions set and clear an interrupt enable flip-flop IEN .


Program Interrupt:

- The computer keeps checking the flag bit, and when it finds it set, it initiates an information transfer.
- The difference of information flow rate between the computer and that of the input—output device makes this type of transfer inefficient.
- An alternative to the programmed controlled procedure is to let the external device inform the computer when it is ready for the transfer.
- In the meantime the computer can be busy with other tasks. This type of transfer uses the interrupt facility.
- While the computer is running a program, it does not check the flags.
- When a flag is set, the computer is momentarily interrupted from the current program.
- The computer deviates momentarily from what it is doing to perform of the input or output transfer.
- It then returns to the current program to continue what it was doing before the interrupt.
- The interrupt enable flip-flop IEN can be set and cleared with two instructions.
 - When IEN is cleared to 0 (with the IOF instruction), the flags cannot interrupt the computer.
 - When IEN is set to (with the ION instruction), the computer can be interrupted.
- The way that the interrupt is handled by the computer can be explained by means of the flowchart of Fig. 5-13.
- An interrupt flip-flop R is included in the computer. When $R = 0$, the computer goes through an instruction cycle.
- During the execute phase of the instruction cycle IEN is checked by the control.
- If it is 0, it indicates that the programmer does not want to use the interrupt, so control continues with the next instruction cycle.
- If IEN is 1, control checks the flag bits. If both flags are 0, it indicates that neither the input nor the output registers are ready for transfer of information. In this case, control continues with the next instruction cycle.
- If either flag is set to 1 while $IEN = 1$, flip-flop R is set to 1. At the end of the execute phase, control checks the value of R , and if it is equal to 1, it goes to an interrupt cycle instead of an instruction cycle.

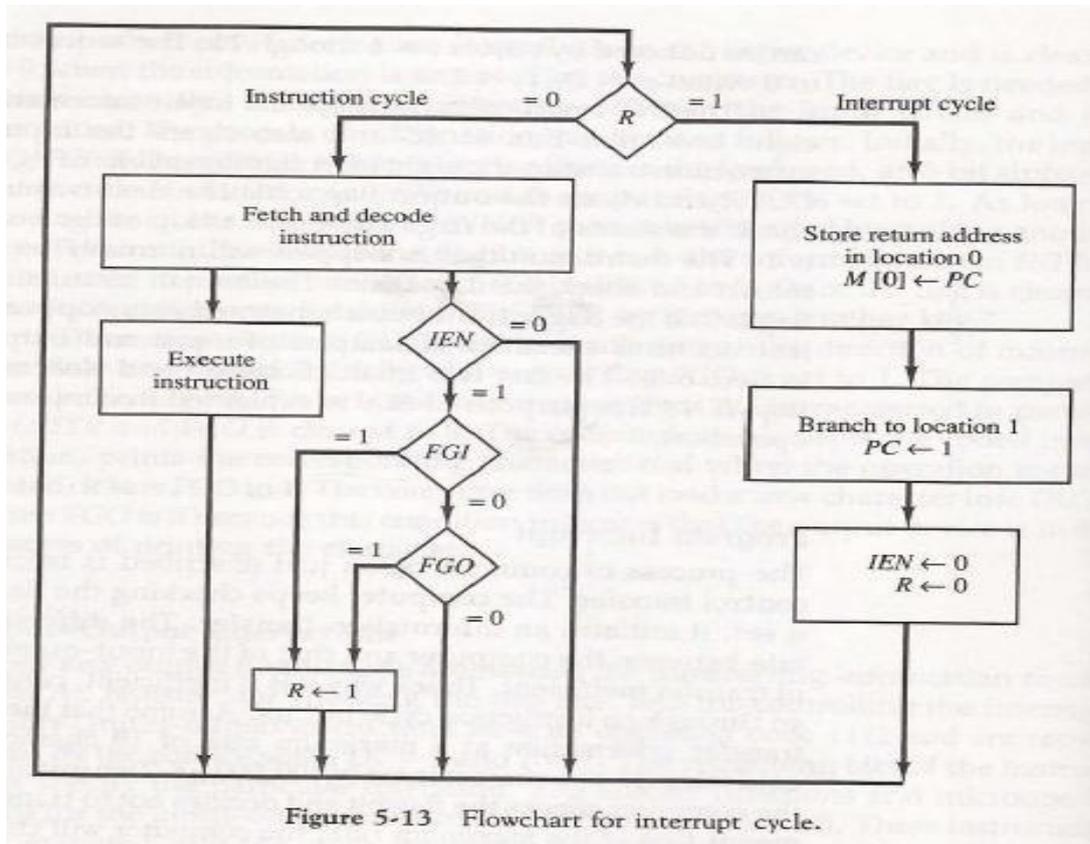

Interrupt cycle:

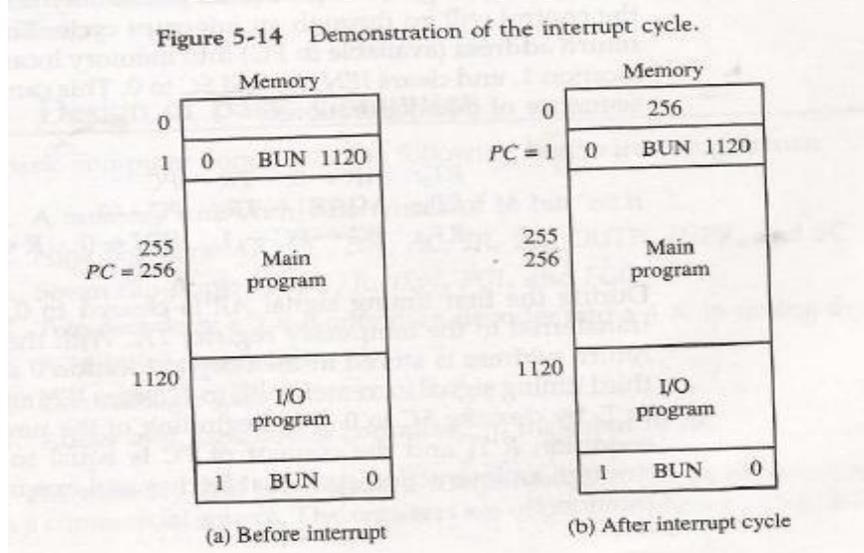- The interrupt cycle is a hardware implementation of a branch and save return address operation.
- The return address available in PC is stored in a specific location.
- This location may be a processor register, a memory stack, or a specific memory location.
- An example that shows what happens during the interrupt cycle is shown in Fig. 5-14.



- When an interrupt occurs and R is set to 1 while the control is executing the instruction at address

255.

- At this time, the returns address 256 is in PC.
- The programmer has previously placed an input—output service program in memory starting from address 1120 and a BUN 1120 instruction at address 1. This is shown in Fig. 5.14(a).
- When control reaches timing signal T_0 and finds that $R = 1$, it proceeds with the interrupt cycle.
- The content of PC (256) is stored in memory location 0, PC is set to 1, and R is cleared to 0.
- The branch instruction at address 1 causes the program to transfer to the input—output service program at address 1120.

- This program checks the flags, determines which flag is set, and then transfers the required input or output information.
- Once this is done, the instruction ION is executed to set IEN to 1 (to enable further interrupts), and the program returns to the location where it was interrupted.